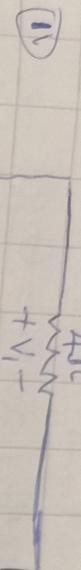


NELSON = ΔV



$$\text{Solution}$$

Using Ohms Law

$$R_{\text{total}} = R_1 + R_2$$

$$= 4 + 2 = 6\Omega$$

$$\text{Total Voltage} = 32 - 8 = 24V$$

$$V = iR \Rightarrow 24 = 6 \times I$$

$$24 = 6I \Rightarrow I = \frac{24}{6}$$

$$I = 4A$$

Voltage across 5Ω $V_b = 5I$
Then applying Kirchhoff's Voltage Law
Sum of voltage rise or drop around the loop equal to 0
 $\therefore 70 - V_x - 2V_x - V_b = 0$
 $70 - 3V_x - 5I = 0$
 $70 - 30I - 5I = 0$
 $70 = 35I$
 $I = \frac{70}{35} = 2A$


Finding V_x and V_b

$$V_x = 10I = 10 \times 2 = 20V$$

$$V_b = 5I = 5 \times 2 = 10V$$

$$V_1 = iR \Rightarrow 4 \times 4 = 16V$$

$$V_2 = 4 \times 2 = 8V$$

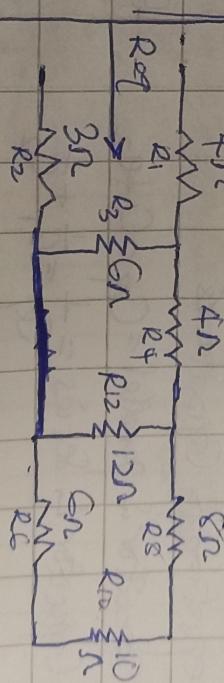

Solution

Finding the equivalent resistance
Req between the two left terminals.

After 3 resistor in series of right

$$R = R_8 + R_9 + R_{10} = 8 + 10 + 5 = 24\Omega$$

Step 2: Combine 24Ω with 12Ω (right)

$$\text{Voltage across } 10\Omega \quad V_x = 10I$$

Solution

$$R = R_4 \times R_2 = \frac{24 \times 12}{24 + 12} = \frac{288}{36} = 8\Omega$$

Step 3: Add 4n with 5n (solutions in series)
 $R = R_4 + R_2 = 4n + 5n = 12n$

Step 4: Combine 12n with 6n (II)

$$R = \frac{12 + 6}{12 + 6} = \frac{18}{18} = 4n$$

Final step: $R_{eq} = 4n + 4n + 3n = 11n$

Step 3: Combine 40nF with 20nF (parallel connection)
 $C = 40\text{nF} + 20\text{nF} = 60\text{nF}$

$$\frac{1}{t} = \frac{1}{120} + \frac{1}{60} = \frac{1+2}{120} = \frac{3}{120} = 25\text{Hz}$$



$$C_p = \frac{1}{\frac{1}{C}} = \frac{3}{120} \Rightarrow 3C = 120$$

$$V_1 = 15$$

$$C = \frac{120}{3} = 40\text{nF}$$

$$C_{eq} = 40\text{nF}$$

$$V_1$$

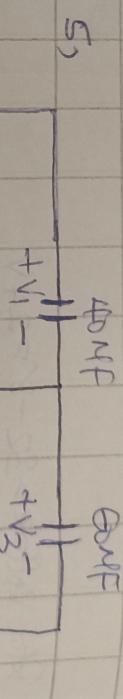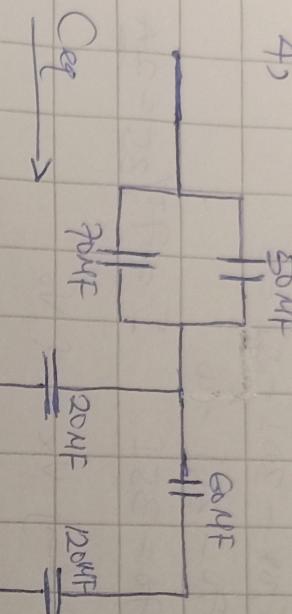

$$V$$

~~equat~~ Solution

equation for C_{eq} parallel

Capacitor in parallel = $C_{eq} = C_1 + C_2$

Capacitor in series = $\frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2}$

finding voltage across each of the Capacitors
 Solution:

Step 1: Add 60nF with 30nF (series connection)

Step 1: Combine 5n with 4n (parallel connection)

(el Capacitors)

$$C = 5n + 4n = 12n$$

Step 2:

Step 2: Add 60nF and 12n (series connection)

Connection)

$$t = \frac{1}{60} + \frac{1}{120} = \frac{2+1}{120} = \frac{3}{120}$$

$$3c = 120 \quad C = \frac{120}{3} = 40\text{nF}$$

Step 2:

Add C_{eq} and 20nF (parallel connection)

$$C_{eq2} = 20\text{nF} + 40\text{nF} = 60\text{nF}$$

Step 3: Combine C_{eq2} with 40nF (series connection)

$$C_{total} = \frac{q_0 \times q_0}{40 + q_0} = 20 \text{ nF}$$

Step 1: Add the 20H and 10H (as Connection)

~~L_{eq}~~ Inductance equation

Step 4: finding V₁ and V₂

Since top capacitor (40nF) is equal to C_{eq2} (40nF), the 10V source split into two equal parts

$$\therefore \frac{10V}{2} = 5V$$

$$V_1 = 5V \quad V_2 = 5V$$

Step 5: finding V₃ and V₄ using


voltage divider

$$V_3 (60 \text{ nF}) = V_{total} \times \frac{C}{C_3 + C_4}$$


$$= 75 \times \frac{1}{3} = 25V$$

$$V_4 (30 \text{ nF}) = \frac{C}{C_3 + C_4} = \frac{2}{3} \times \frac{60}{60 + 30} = 20V$$

$$L_{eq} = 75 \times \frac{2}{3} = 50H$$

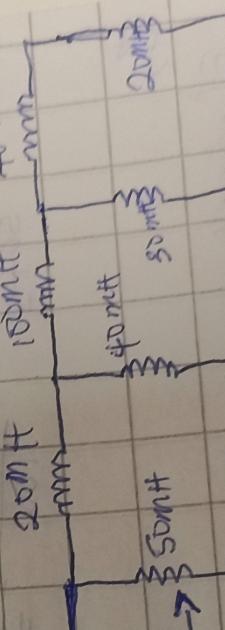

$$L_{eq} \rightarrow$$

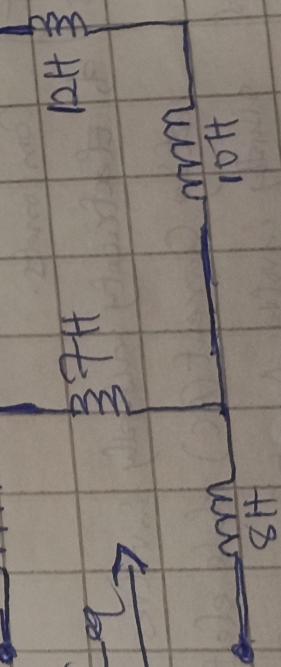

Finding Inductance equivalent
solution - Step 1

$$Add A 10mH and 20mH (series connection)$$

$$L_{eq} = 10mH + 20mH = 30mH$$

Solution

Step 2: Combine 20mH and 30mH (parallel connection)

$$L_{parallel} = \frac{60 \times 30}{60 + 30} = \frac{1800}{90} = \underline{\underline{20\text{mH}}}$$

Step 3: Add 100mH and 20mH (series connection)

$$L_{right} = 100\text{mH} + 20\text{mH} = \underline{\underline{120\text{mH}}}$$

Step 4: Combine 120mH and 40mH (parallel connection)

$$L_{parallel} = \frac{120 \times 40}{120 + 40} = \frac{4800}{160} = \underline{\underline{30\text{mH}}}$$

Step 5: Add 30mH and 20mH (series connection)

$$L_{right} = 30\text{mH} + 20\text{mH} = \underline{\underline{50\text{mH}}}$$

Final Step: Combine 50mH and Vertical 50mH to get L_{eq} (parallel connection)

$$\therefore L_{eq} = \frac{50 \times 50}{50 + 50} = \frac{2500}{100} = \underline{\underline{25\text{mH}}}$$

as light, heat, mechanical motion etc while Electronic devices controlling the flow of electrons to perform specific tasks such as amplifying signals processing data or switching.

it uses transistors and microchips as its components to manipulate electrical current. eg smartphone, computer, microphone.

Different between electric current and electronics :

- a) Electricity transmits power while electronics transmit information.

b) Electricity uses conductor as medium for transmission while electronics uses semi-conductors.

c) Electricity uses resistors, capacitors and inductors as its components while electronics uses transistors, diodes and integrated circuit as its components.

Electricity is the flow or passage of electrons through a conductor such as a copper wire to transmit electrical power. Its aims of covering electrical energy into other forms of energy such as, electricity is typically high voltage level while electronic is typically low voltage level.

Q. Using Smart Thermostat to explain how electronics contribute.

The explanation of how electronics contribute to the functionality of Smart Thermostat. Smart thermostat function as an intelligent system where electronics bridge the gap between physical data and electrical power. Thermistors first sense the environmental changes by translating temperature into variable resist once. This data is processed by a microcontroller, the System's brain which uses programmed logic to decide when to activate the HVAC system. To protect this sensitive processor, capacitors filter the power supply to ensure a smooth smooth, noise free voltage. When activation is required, the microcontroller triggers transistors to act as electronic switches, safely engaging high power connections to the AC. Simultaneously, inductors in the Wi-Fi modules trans radios frequencies to enable wireless communication with internet.

Ans 10,

Scope of Electricity and Electronics with their Applications

Electricity involves the generation, distribution and utilisation of electrical power to perform physical work. It primarily deals with high voltage systems and the conversion of energy into light, heat etc. Applications include power grid, industrial motors, heating and lighting, renewable energy etc.

Electronics involves the precise manipulation of low voltage currents to process, store, and transmit information. It relies on semi-conductor materials and active components such as transistors to create logical decisions within a circuit. Applications are: Computing and IT, telecommunications, IoT and smart devices, medical electronics etc.